

TB141110

Reg.No:

Name:

B.Sc. DEGREE (C.B.C.S.S) EXAMINATION, NOVEMBER 2014

B.Sc. COMPUTER APPLICATIONS - FIRST SEMESTER

CORE PAPER - 1

CA1FDS – FUNDAMENTALS OF DIGITAL SYSTEMS

Time: 3 Hours

Maximum Marks: 80

Part A

Answer all questions. Each question carries 1 mark.

1. The binary number that follows 1011 is
a) 1111 b) 1110
c) 1100 d) 1101
2. The hexadecimal number system has a base of
a) 4 b) 8
c) 10 d) 16
3. Which of the following is correct?
a) $A.A=1$ b) $A+1=A$
c) $A.1=A$ d) $A+A'=0$
4. The output of a ----- gate is 0 when at least one input is 1.
a) NAND b) NOR
c) XOR d) AND
5. When both inputs of a JK flip flop are high, and the clock cycles, the output will -----.
a) be invalid b) not change c) remains unchanged d) toggle
6. A circuit with one input and many outputs is called a -----.
7. ----- is an example for a combinational circuit.
8. Asynchronous counters are also called -----.
9. ----- is the abbreviation for binary digit.
10. PROM stands for -----.

(10 x 1 = 10)

Part B

Answer any eight questions in one or two sentences. Each question carries 2 marks.

11. Convert $(27)_8$ to binary.
12. What is sign magnitude form?
13. What do you mean by BCD numbers?
14. Perform $11001 - 110$ in 2's complement method.

(P.T.O)

15. Explain NAND gate.
16. What do you mean by don't care conditions?
17. Prove that $A + AB = A$.
18. What is an encoder?
19. What is the use of DMUX?
20. What is a D-flip flop?
21. What is a shift register?
22. Differentiate between RAM and ROM.

(8 x 2 = 16)

Part C

Answer any six questions in 50 words each. Each question carries 4 marks.

23. Discuss the steps to convert a hexadecimal number to octal equivalent. Convert $(AC.2B)_{16}$ to binary.
24. Perform the following additions in BCD:
 - a) $(45)_{10} + (27)_{10}$
 - b) $(81)_{10} + (35)_{10}$
25. Explain SOP and POS expressions.
26. Show that NOR gate is a universal gate.
27. Simplify using K-Map: $F(A, B, C, D) = (1, 2, 3, 8, 9, 10, 11, 14, 15)$
28. Differentiate between half adder and full adder.
29. Construct an 8×1 MUX.
30. Explain the working of a simultaneous A/D converter.
31. List the various types of ROM.

(6 x 4 = 24)

Part D

Answer any two questions in 100 words. Each question carries 15 marks.

32. Explain popular positional number systems in detail.
33. State and prove De-Morgan's theorems.
34. Explain the working of a synchronous BCD counter with a diagram.
35. Explain PIPO and SIPO shift registers in detail.

(2 x 15 = 30)